
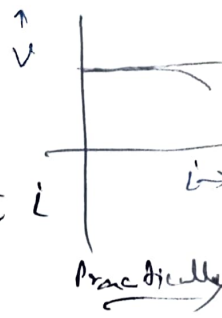
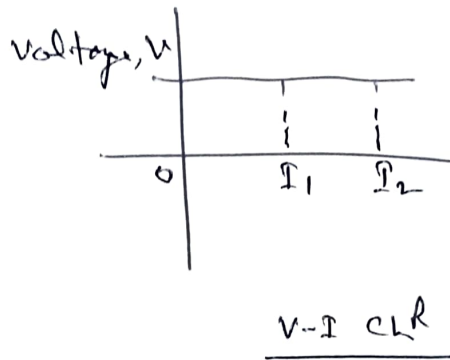


# UNIT-I
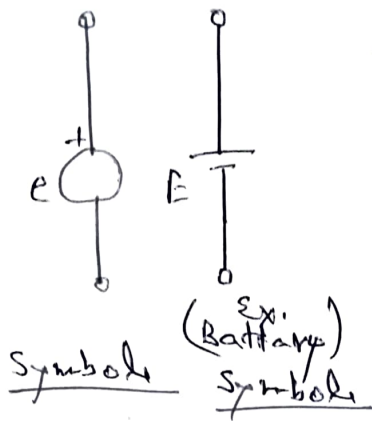
## DC Ckt Analysis & Network Theorems

→ Ident Independent Current & Voltage Sources (By Del Toro)

- Ident Independent Voltage Source - is that in which the value of the voltage is not dependent on the either the magnitude or direction of current flowing through the source.




→ Ideal voltage source has zero internal resistance

By Ohm's law  $R = \frac{\Delta V}{\Delta I} = \frac{V_2 - V_1}{I_2 - I_1} = \frac{0}{I_2 - I_1} = 0$

- Ideal Current Source - → so replaced by short ckt.

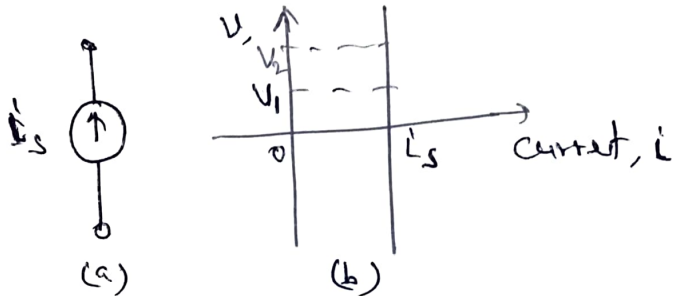- supplies specified current independent of value & direction of the voltage appearing across its terminals.




→ Ideal Current Source - internal resistance is infinite


$$R = \frac{\Delta V}{\Delta I} = \frac{V_2 - V_1}{0} = \infty$$

→ so replaced by open ckt.

→ Dependent Source -

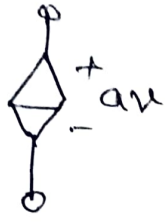

Voltage dependent  
Voltage source

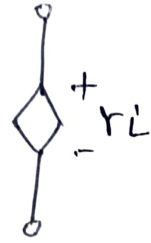

Current dependent  
voltage source



voltage depd  
current  
source



current depd  
current source

→ Active Elements -

- Independent source which can deliver or absorb energy continuously.

Ex - Ideal Voltage & Current sources

Voltage source - Battery, DC Gen, AC Gen; Current source - Photo-electric cells, Molybdenum Gen.

→ Passive Elements -

- Components which dissipate or store energy.

Ex - R, L, C.


CRT. Parameter

-> Resistance - (R) - Property of a substance which opposes the flow of electricity through it.

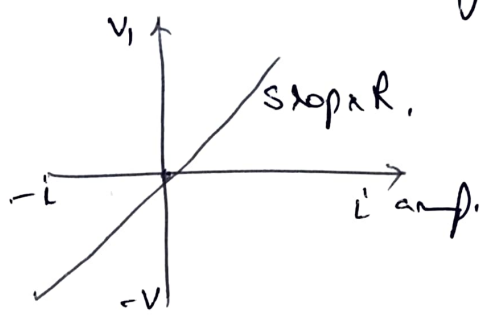a) CRT V-I Graph -

By Ohm's law  $R = \frac{V}{I} \Omega$  - (1)

- Above Eqn is a linear algebraic expression when the proportionality factor R is independent of current.



- Experiment shows that the resistance of most metallic conductors varies with temp.

$R_2 = R_1 [1 + \alpha_1 (T_2 - T_1)]$

-  $\alpha_1$  - temp coefficient of resist at  $T_1$ , in  $^{\circ}C$ .

b) Energy V-I Graph -

power absorbed by resistor -

$P = VI = (IR)I = I^2R$

Energy -  $W = I^2RT$  Joule

c) Geometrical V-I Graph -

$R = \frac{\rho l}{A} \Omega$

l -> length of conductor (m)

A -> Area of cross-section ( $m^2$ )

$\rho$  -> resistivity of the material ( $\Omega m$ )

-> Conductance  $G = \frac{1}{R}$


-> physical aspects - colour code

## ② Inductance -

- Inductance can be characterised as the property of a ckt element by which energy is capable of being stored in a magnetic flux field.
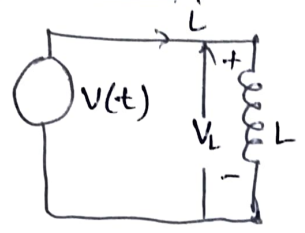
### Ckt View Point

$$v_L = L \frac{di}{dt} \quad \text{--- ①, } v_L \text{ \& } i \text{ are fun. of time.}$$



$$L = \frac{v_L}{di/dt} \quad \text{volt-seconds or } \underline{\text{henry}} \text{ or } \text{--- ② } \text{amp.}$$

$$i(t) = \frac{1}{L} \int_0^t v_L dt + i(0) \quad \text{--- ③}$$

Eqs ① & ③ shows, the current in an inductor can't change abruptly in zero time.


### Energy View Point

$$W = \frac{1}{2} L i^2$$

Energy stored in magnetic form.

### Geometrical View Point

$$L = N \frac{d\phi}{di}$$

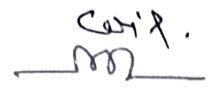

$$\text{or } L = \frac{N\phi}{i} = \frac{Wb-t}{A}$$

N → No. of turns  
ϕ → flux  
i → current

③ Capacitance

q & V via P

$q = CV_c$  - ①

$i = \frac{dq}{dt} = C \frac{dV_c}{dt}$  A - ②

$C = \frac{i}{\frac{dV_c}{dt}}$  - ③

amp-sec / volt / coulomb / volt  
farad.

$V_c = \frac{1}{C} \int_0^t i dt$



b) Energy via P

it stores energy in electro static form

$W = \frac{1}{2} CV^2$  J

c) Geometric

$C = \epsilon \frac{A}{d}$  F

A → Area of plates

d → distance b/w plates

ε → permittivity of dielectric material.

UNIT - I  
2. Network Theory

③ NT

Linear  
→ Resistive elements for which  $V-I$  char is straight line.

Linear CKT - Electric CKT containing only linear Resistance

Non Linear -

→ Resistive elements for which  $V-I$  char is other than a straight line.

Non linear CKT - so electric CKT containing them (non linear elements) as tungsten element, vacuum tubes and transistor etc

Bilateral CKT - An electric CKT, whose char or properties are same in either direction (as Distribution & Transmission line)

Unilateral CKT - An electric CKT, whose char or properties change with direction of its operation (as diode rectifier)

Passive Network - Network containing no source of emf in it.

Active Network - Network containing one or more sources of emf

One Part Network - Part electric network when a branch is removed from it and left with a pair of terminals.

Two Part Network → when two branches removed, so that network is left with four terminals (or two pairs of terminals), so remainder network is called Two Part Network.

Mesh ~~enclosed~~ - Electric network may provide a single closed path.

Junction (Node) - A point in a network where two or more branches meet.

Branch - Any section which joins two nodes, without passing through a third node.

Loop - A closed path in a network formed by a number of connected branches.

→ Mesh is a loop that contains no other loop within it.

→ KCL → First Law


→ The algebraic sum of currents flowing towards a junction in an electric ckt is zero.

→ The sum of currents flowing towards any junction is equal to the sum of currents flowing away from junction.

$$\boxed{\sum I = 0} \rightarrow i_1(t) + i_2(t) + i_4(t) = i_3(t)$$

$$I_1 + I_2 - I_3 + I_4 = 0$$

or  $I_1 + I_2 + I_4 = I_3$

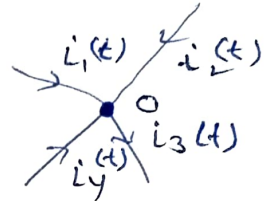

In Comp Current  
= Out going Currents

→ KVL → Second Law

→ In any closed circuit or mesh, the algebraic sum of all electromotive forces (e.m.f's) and the voltage drops is equal to zero.


i.e. In any closed circuit or mesh -

Algebraic sum of e.m.f's  
+ Algebraic sum of voltage drops  
= 0

$$\boxed{\sum IR + \sum E = 0}$$


Sign Convention

Rise in Potential


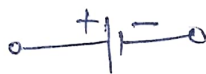


←  
Positive  
(+)

Fall in Potential

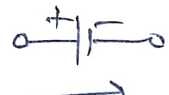


→  
Negative  
(-)

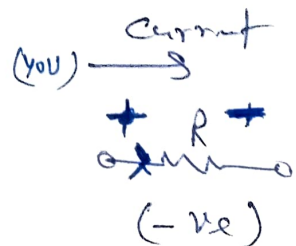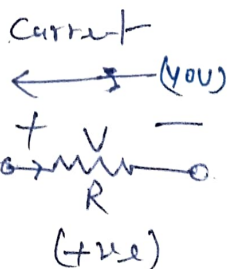

→ Mesh Current Method / Loop Current / Mesh analysis  
Maxwell's mesh current method consists of following steps-

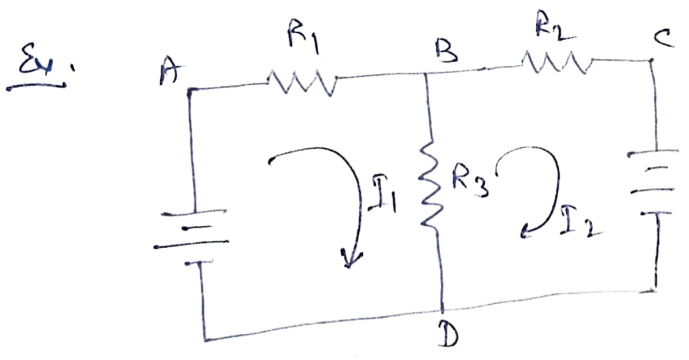- i) Each mesh is assigned a separate mesh current. For convenience, all mesh currents are assumed to flow in clockwise direction.
- ii) If two mesh currents are flowing through a circuit element, the actual current in the circuit element is the algebraic sum of two.
- iii) KVL is applied to write the equation for each mesh in terms of mesh currents.  
Write mesh equation, rise in potential (+)  
fall in potential (-).
- iv) If the value of any mesh current comes out to be negative, it means that true direction of that mesh current is anticlockwise i.e. opposite to the assumed clockwise direction.



→ Numerical Problems.




## Nodal Analysis:-

(5) NT

In this method -

- One of the nodes is taken as the reference node (node - is a point in a network where two or more circuit elements meet)
- The potentials of all points in the circuit are measured w.r.t this reference node.
- Apply KCL to write the equations & solve them.
- Then each branch current can be determined because voltage across each element will be known.

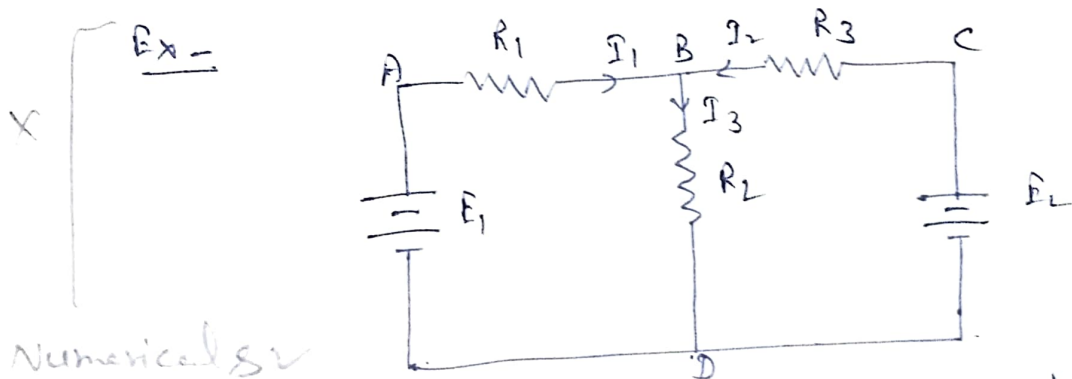\* Hence nodal analysis essentially aims at choosing a reference node in the network and then finding the unknown voltages at nodes w.r.t. reference node.



If we can find  $V_B$ , then all currents  $I_1, I_2, I_3$  can be determined as given below -

In mesh ABDA, the voltage drop across  $R_1$  is  $E_1 - V_B$ .

$$\therefore I_1 = \frac{E_1 - V_B}{R_1}$$

In mesh BCDB, the voltage drop across  $R_3$  is  $E_2 - V_B$ .

$$\therefore I_2 = \frac{E_2 - V_B}{R_3}$$


$$\& I_3 = \frac{V_B}{R_2}$$

4. By KCL at node B point -

$$I_1 + I_2 = I_3$$

only  $V_B$  is

### - Voltage Dividing Rule :-

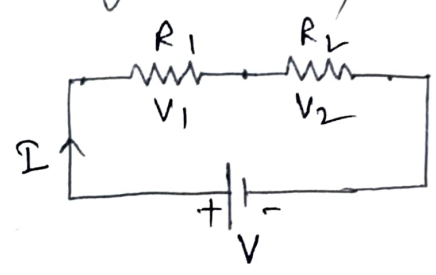

Eqn. or Total Resistance

$$R = R_1 + R_2$$

$$I = \frac{V}{R} = \frac{V}{R_1 + R_2}$$


$$V_1 = I R_1 = \frac{V}{R_1 + R_2} \cdot R_1$$

$$V_1 = V \cdot \frac{R_1}{R_1 + R_2}$$

$$V_2 = I R_2 = \frac{V}{R_1 + R_2} \cdot R_2 \Rightarrow$$

$$V_2 = V \cdot \frac{R_2}{R_1 + R_2}$$

### - Current Dividing Rule :-

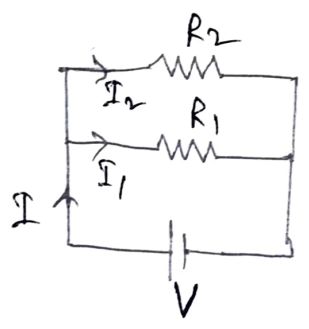

Total Resistance

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$V = I \cdot R = I \cdot \frac{R_1 R_2}{R_1 + R_2}$$

$$\Rightarrow \therefore I_1 = \frac{V}{R_1} = \frac{I \cdot R_1 R_2}{R_1 (R_1 + R_2)} =$$


$$I_1 = I \cdot \frac{R_2}{(R_1 + R_2)}$$

$$\Rightarrow \therefore I_2 = \frac{V}{R_2} = \frac{I \cdot R_1 R_2}{R_2 (R_1 + R_2)}$$

$$I_2 = I \cdot \frac{R_1}{R_1 + R_2}$$

- Source "Transformation" !!
- Source can either operate as a current source or voltage source.
- If load impedance is very large in comparison to internal impedance, we voltage source.
- If load impedance is very small in comparison to internal impedance of source, it is better to represent source as a current source.
- It is possible to convert a voltage source into a current source or vice-versa. (1)

Ex.

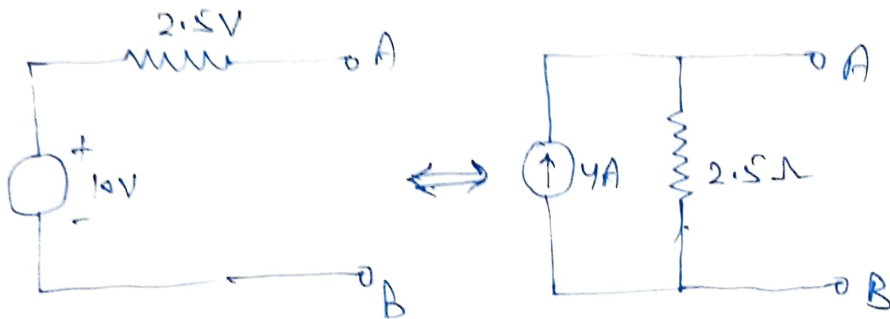

## Om. Theorem

### Super Position

The basic principle of superposition states that, if the effect produced in a system is directly proportional to the cause, then the overall effect produced in the system, due to a number of causes acting jointly, can be determined by superposition (adding) the effects of each source acting separately.

- ✓ In a linear network containing more than one sources, the resultant current in any branch is the algebraic sum of the currents that would be produced by each source acting alone (all other sources would be replaced meanwhile by their respective internal resistances).
- ✓ The Superposition theorem is only applicable to linear networks and systems. We can call a device linear, if it is characterised by an equation of the form -

$$y = mx + c \quad \text{where } m \text{ is a constant and not a function of } x.$$

The principle of superposition is useful for linearity test of the system.

This is not valid for power relationships.

Sources can be made inoperative by

- short-circuiting the voltage sources and replacing them by their series impedances.
- open-circuiting the current sources and substituting them by their shunt impedances.

A linear network comprises independent sources, linear dependent sources and linear passive elements like resistors, inductor, capacitor and transformer. Moreover, the components may either be time-varying or time invariant.


A linear ckt is one whose parameters (e.g. resistances) are constant, they do not change with current & voltage.

→ Thevenin Theorem :-

- This theorem provides a mathematical technique for replacing a two terminal network.
- It states that - Any linear, active, bilateral two terminal network can be replaced by a voltage source  $V_{th}$  in series with a resistance  $R_{th}$  (or  $Z_{th}$  in ac ckt), where

$V_{th}$  - Thevenin voltage or open ckt voltage across two terminal (load terminal) when load is disconnected.

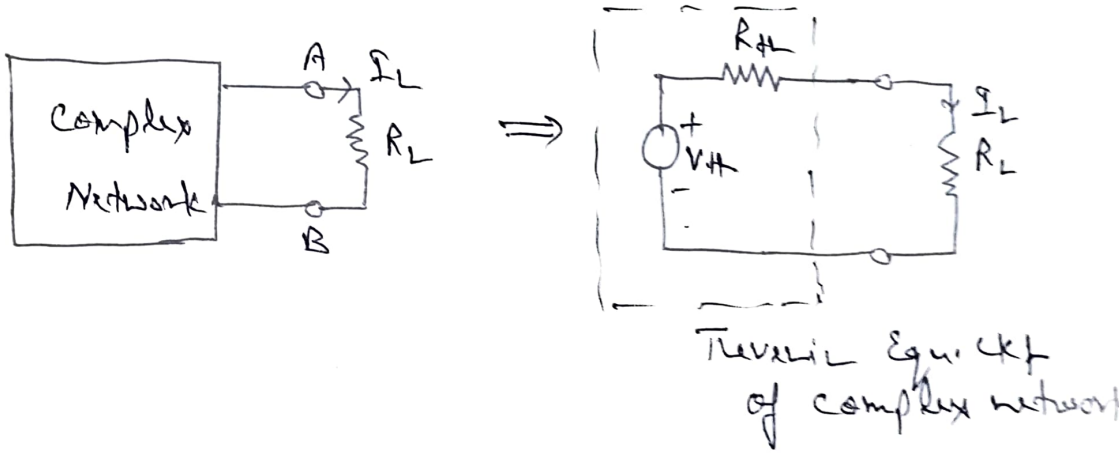$R_{th}$  - Thevenin eq<sup>n</sup> resistance of network across two terminal, replacing all sources with their internal resistance. (with load disconnected)



load current

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

✓  
→ Norton Theorem :-

- By using this theorem we can replace a complex network by a current source in parallel with a resistance.

- Any linear, active, bilateral complex network can be replaced by a current source  $I_N$  in parallel with a resistance  $R_N$ .


Where  $I_N =$  Short ckt current between two terminal  $I_N = I_{sc}$

$R_N =$  Equi. Norton resistance of complex network across two terminal, replace all the sources by their internal resistances.

$R_N = R_{th}$

Load Current  $I_L = I_N \cdot \frac{R_N}{R_N + R_L}$

$I_{sc} = I_N = \frac{V_{th}}{R_{th}}$

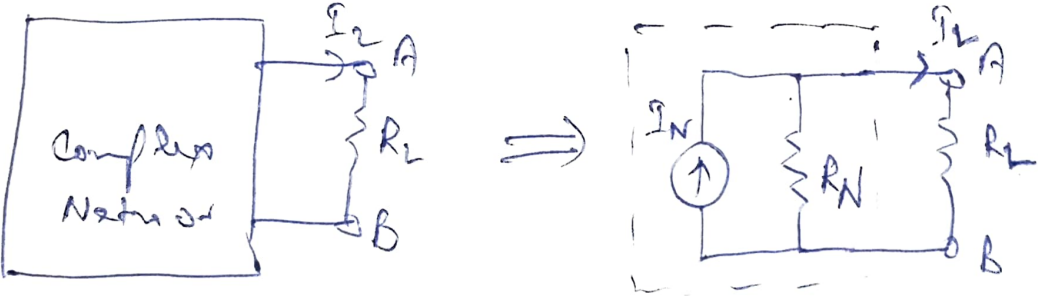


⇒ Max. Power Transfer Theorem:-


MAT theorem for dc networks is stated as:-

A load resistance connected to a dc network abstracts/draws max. power when load resistance is equal to equivalent resistance of the network as seen from load terminals.

Proof:-

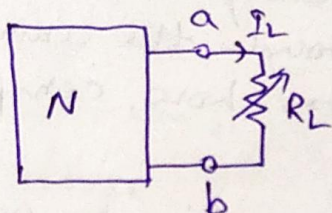

DC Network, N with RL

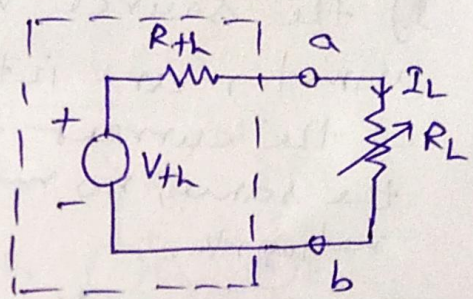

Thevenin Eqn Network

$$I_L = \frac{V_{th}}{R_{th} + R_L} \quad \text{--- (1)}$$

Power delivered to load,  $P_L = I_L^2 R_L \quad \text{--- (2)}$

By (1) + (2)  $\Rightarrow P_L = \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 \cdot R_L$

$$P_L = \frac{V_{th}^2 \cdot R_L}{R_{th}^2 + R_L^2 + 2R_{th}R_L} = \frac{V_{th}^2}{\frac{R_{th}^2}{R_L} + R_L + 2R_{th}}$$

for max. power  $P_L$ , denominator

$x = \frac{R_{th}^2}{R_L} + R_L + 2R_{th}$  should be min.

$$\frac{dx}{dR_L} = -\frac{R_{th}^2}{R_L^2} + 1 + 0$$

$$0 = -\frac{R_{th}^2}{R_L^2} + 1$$

$$\boxed{R_L = R_{Th}} \quad \text{Proved.}$$

$$\text{Max. Power, } P_{max} = \frac{V_{Th}^2 \cdot R_{Th}}{(R_{Th} + R_{Th})^2} = \frac{V_{Th}^2 \cdot R_{Th}}{4R_{Th}}$$

$$\boxed{P_{max} = \frac{V_{Th}^2}{4R_{Th}}}$$

### Reciprocity Theorem!

- According to this theorem -

If the source voltage and zero-resistance ammeter are interchanged, the magnitude of the current through the ammeter will be the same, no matter how complicated the network.


- In other words, In a linear passive network, supply voltage  $V$  and current  $I$  are mutually transferable.

The ratio of  $V$  and  $I$  is called the transfer resistance (transfer impedance in AC system).

→ Limitation! - It is applicable only to single-source networks and not in multi-source networks.



# Star Delta Transformation

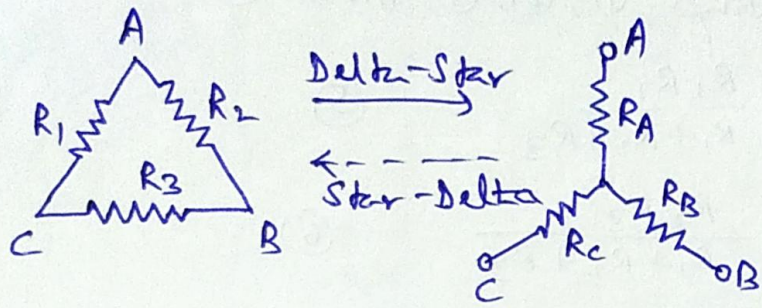

Delta-Star Tr - The replacement of delta (mesh) by equivalent star system is known as delta-star Tr.

- Two systems will be eq. or identical if the resistances measured between any pair of lines is same in both systems, when the third line is open.

Hence Resistance between terminal B & C -

$$R_{BC} = R_3 \parallel (R_1 + R_2) = \frac{R_3 (R_1 + R_2)}{R_1 + R_2 + R_3} \text{ in delta system}$$

and  $R_{BC} = R_B + R_C$  in star system

- Since both systems are identical, resistances measured between terminals B and C in both systems must be equal.

$$\therefore R_B + R_C = \frac{R_3 (R_1 + R_2)}{R_1 + R_2 + R_3} \quad \text{--- (1)}$$

Similarly  $R_C + R_A = \frac{R_1 (R_2 + R_3)}{R_1 + R_2 + R_3} \quad \text{--- (2)}$

$$R_A + R_B = \frac{R_2 (R_1 + R_3)}{R_1 + R_2 + R_3} \quad \text{--- (3)}$$

Adding (1), (2), (3) ---

$$2(R_A + R_B + R_C) = \frac{2(R_1 R_2 + R_2 R_3 + R_3 R_1)}{R_1 + R_2 + R_3} \quad \text{---}$$

$$R_A + R_B + R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1 + R_2 + R_3} \quad \text{--- (4)}$$

→ Subtracting ①, ②, ③ from ④ -

$$R_A = \frac{R_1 R_2}{R_1 + R_2 + R_3} \quad \text{--- ⑤}$$

$$R_B = \frac{R_2 R_3}{R_1 + R_2 + R_3} \quad \text{--- ⑥}$$

$$R_C = \frac{R_3 R_1}{R_1 + R_2 + R_3} \quad \text{--- ⑦}$$

If  $R_1 = R_2 = R_3 = R_D$  then  $R_A = R_B = R_C = R_S$

$$R_S = \frac{R_D R_D}{R_D + R_D + R_D} = \frac{R_D}{3}$$

Star-Delta Tr - Multiplying ⑤ & ⑥ and ⑤ & ⑦ and ⑦ & ⑤ and adding them -

$$\begin{aligned} R_A R_B + R_B R_C + R_C R_A &= \frac{R_1 R_2^2 R_3 + R_1 R_3^2 R_2 + R_1^2 R_2 R_3}{(R_1 + R_2 + R_3)^2} \\ &= \frac{R_1 R_2 R_3 (R_2 + R_3 + R_1)}{(R_1 + R_2 + R_3)^2} \end{aligned}$$

$$\boxed{R_A R_B + R_B R_C + R_C R_A = \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}} \quad \text{--- ⑧}$$

Dividing ⑤, ⑥, ⑦ from ⑧ -

$$R_3 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A} = R_B + R_C + \frac{R_B R_C}{R_A} \quad \text{--- ⑨}$$

$$R_1 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B} = R_A + R_C + \frac{R_A R_C}{R_B} \quad \text{--- ⑩}$$

$$R_2 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C} = R_A + R_B + \frac{R_A R_B}{R_C} \quad \text{--- ⑪}$$

Again

$$R_D = R_S + R_S + \frac{R_S R_S}{R_S} = 3 R_S$$